



Stellenbosch

UNIVERSITY
IYUNIVESITHI
UNIVERSITEIT

E344 Assignment 1

Henry Louw

23837217

Report submitted in partial fulfilment of the requirements of the module
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical
and Electronic Engineering at Stellenbosch University.

August 7, 2022

Plagiaatverklaring / *Plagiarism Declaration*

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

Plagiarism is the use of ideas, material and other intellectual property of another's work and to present it as my own.

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

I agree that plagiarism is a punishable offence because it constitutes theft.

3. Ek verstaan ook dat direkte vertalings plagiaat is.


I also understand that direct translations are plagiarism.

4. Dienooreenkomstig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelike aanhaal van teks sonder aanhalingstekens (selfs al word die bron volledig erken) plagiaat is.

Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism.

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.

23837217	
Studentenommer / <i>Student number</i>	Handtekening / <i>Signature</i>
HC. Louw	August 7, 2022
Voorletters en van / <i>Initials and surname</i>	Datum / <i>Date</i>

Contents

Declaration	i
List of Figures	iii
List of Tables	iv
Nomenclature	v
1. Literature survey	1
1.1. Operational amplifiers	1
1.2. Current sensing	3
1.3. Ultrasonic sensors	4
1.4. Converting PWM signals to analogue	5
1.5. Fundamental operation of the range sensor	6
2. Detail design	8
2.1. Voltage regulator	10
2.2. Design for ultrasonic sensor	10
3. Results	12
3.1. Ultrasonic sensor design	15
Bibliography	18
A. Social contract	19
B. GitHub Activity Heatmap	20

List of Figures

List of Tables

3.1. voltage use of circuit when motor:..	12
---	----

Nomenclature

Variables and functions

Acronyms and abbreviations

Op amp operational amplifier

A ampere

s seconds PWM

Pulse Width Voltage
modulation V

Chapter 1

Literature survey

For the first assignment we had to design a current sensing circuit. A current sensing circuit is a circuit that can measure the current as the current is flowing through the circuit. We also had to use a circuit that can cancel all the noise, which is caused by an AC input. We had to amplify a certain signal by designing a circuit which consists of an operational amplifier, a low current sensing circuit and a filter, which will be able to filter out all the noise of the signal.


1.1. Operational amplifiers

Operational amplifiers: limitations and considerations

Operational amplifier configurations


There are two main operational amplifiers that can be used to amplify signals. These two amplifiers are called: inverting amplifier and non-inverting amplifier.

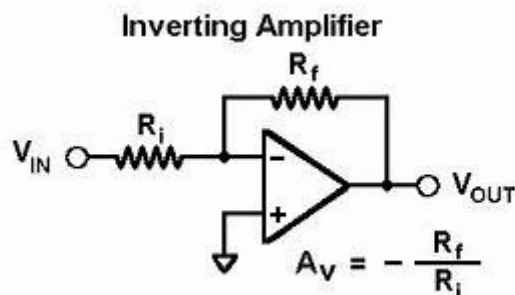Inverting amplifiers are used to amplify a signal where the output signal is fed back to the inverting input through a resistor R_2 . The input signal flows through R_1 to the inverting input. The positive pin is connected to ground. The gain of the circuit will be negative, because of the input being applied to the negative pin. This means that the output signal and the




input signal will be out of phase.

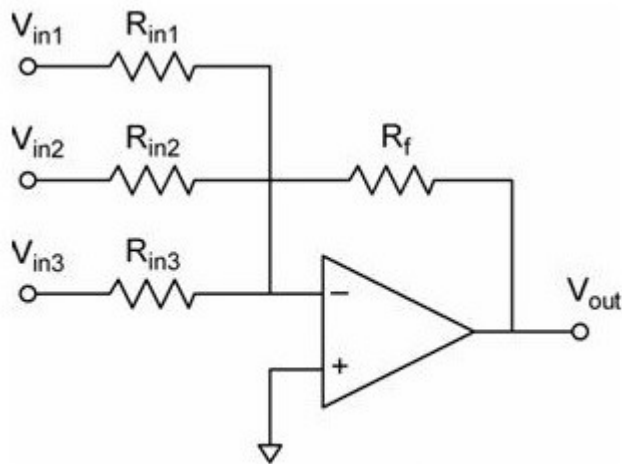An inverting summing amplifier will be an amplifier that has two resistors that will be added in parallel to one another. These two resistors will then be connected to the inverting pin.




The Summing Amplifier Circuit Diagram

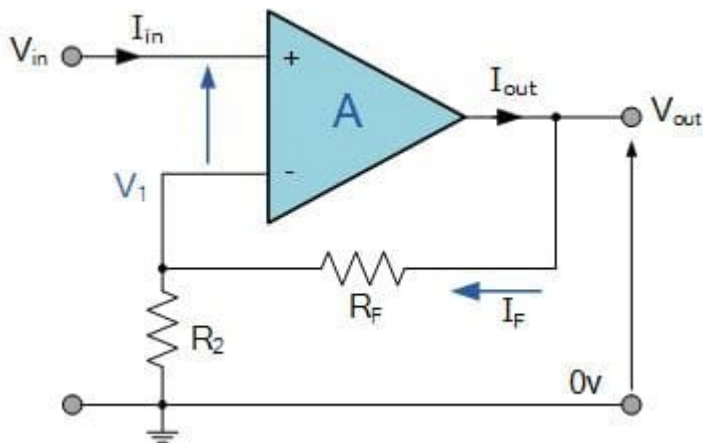Non Inverting amplifier is very similar to the Inverting amplifier. The only main difference is that the voltage input will be connected to the non-inverting pin. The gain will be positive and the output signal and the input signal will be phase and therefore we will be using a non-inverting amplifier.




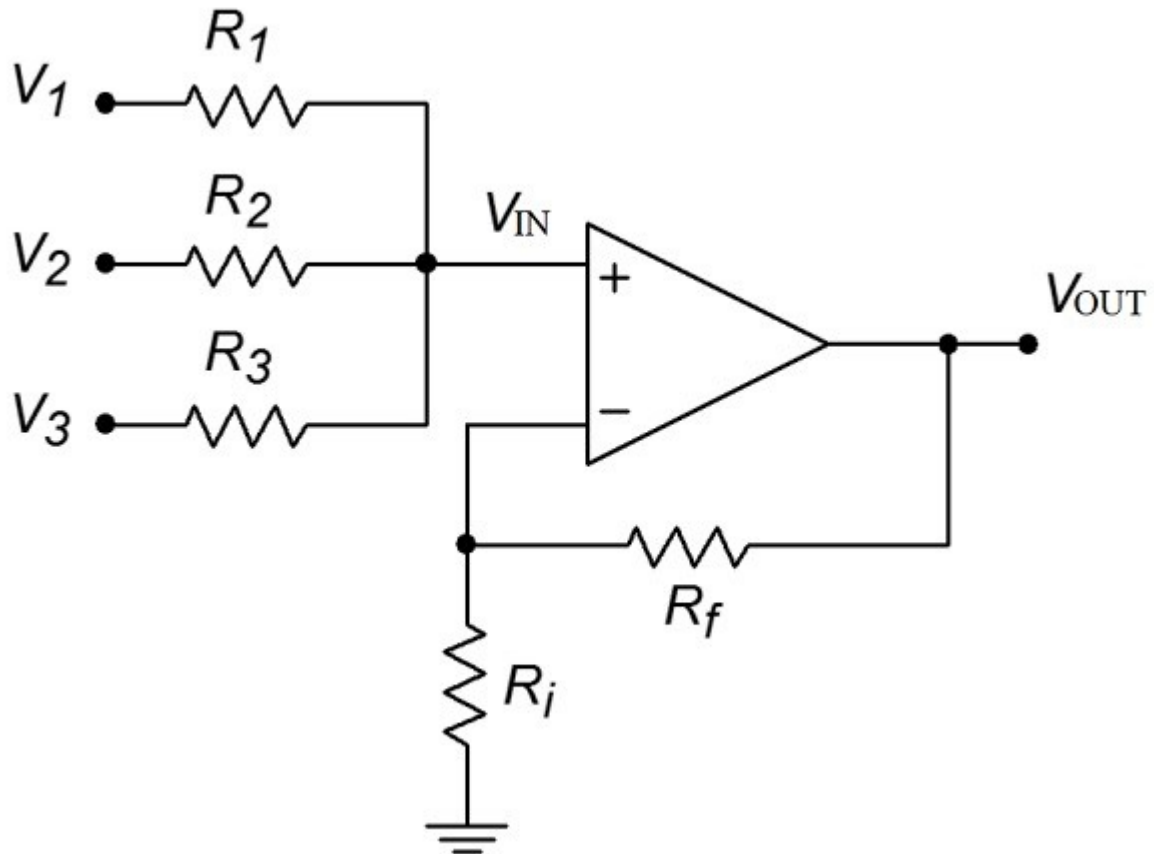
A non-inverting summing amplifier will be an amplifier that has two resistor that will be added parallel to one another. These two resistors will then be connected to the inverting pin.



An amplifier consists of an inverting input(-), a non-inverting input(+), a voltage supply(+), and a negative voltage supply and an output. These components are then used to amplify a signal. The amplifier we will be using is the non-inverting amplifier. We don't want the input signal and the output signal to be out of phase. The gain we will be calculating will be $A_v = (1 + R_f/R_2)$. We will be using an LTC6079 op amp. This op amp doesn't have any range of common mode voltage. This op amp works with PMOS and NMOS pairs. A transition will happen when the common mode voltage is 0.9-1.3V.

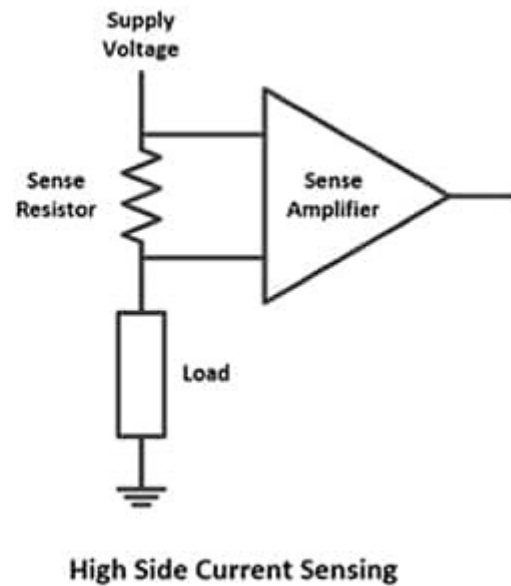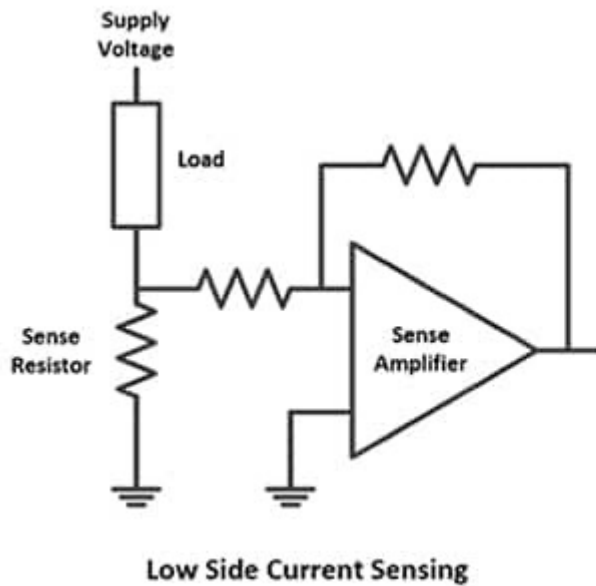1.2. Current sensing

A current sensing circuit is a circuit which is used to measure current. There are two different current sensing circuits called invasive and non-invasive current sensing. A non-invasive current sensor can be placed around a supply line where it will be able to tell you how much current is present. An AC current sensor uses a non-invasive current sensor to measure alternative current. A DC current sensor would only be able to measure DC current. You will also find that there are two current sensing called high side current sensing and low side current sensing. Low side current sensing is when R_{shunt} is connected to ground and to the power supply. High side current sensing is when R_{shunt} is connected to the power supply and the load.



The maximum current flowing through the motor will be 1A. The voltage over the 10m ohm will be 10mV. The power over this particular resistor will then be $p=IV$, which is 10mW.

1.3. Ultrasonic sensors

Ultrasonic sensor are devices that measures distance by sending out ultrasonic signals and converts the reflected signals to electrical signals. Ultrasonic sensors has two main components namely: the transmitter and the receiver. The reason why the ultrasonic sensors send ultrasonic waves is mainly because ultrasonic waves travels faster than audible sound.

To calculate the distance the ultrasonic sensor takes the time the signal travels from the transmitter until the reflected signal is received by the receiver. The formula that is used is:


$$D=0.5T+C$$

D=Distance.

T=Time

C=Speed of sound(343 meters per second) The power specification of the ultrasonic sensor is the following:

Operating Voltage	Min range	Max range	Operating current	Raging accuracy
5V DC	3cm	4m	15mA	3mm

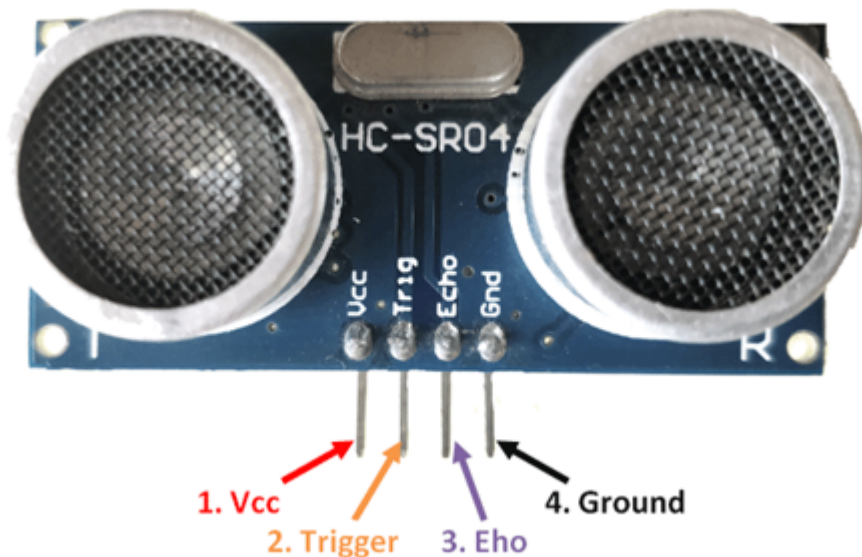

1. The Vcc pin will be supplied with 5V.
2. The trigger pin is used to trigger ultrasonic sound pulses. When this pin is set to HIGH for 10 μ s, the system initiates an ultrasonic burst.
3. The echo pin goes High when ultrasonic burst is transmitted and remain HIGH until it receives an echo. It then goes low. The distance can then be calculated by looking at the time for which the the echo pin stays HIGH.
4. Is just connected to ground.

1.4. Converting PWM signals to analogue

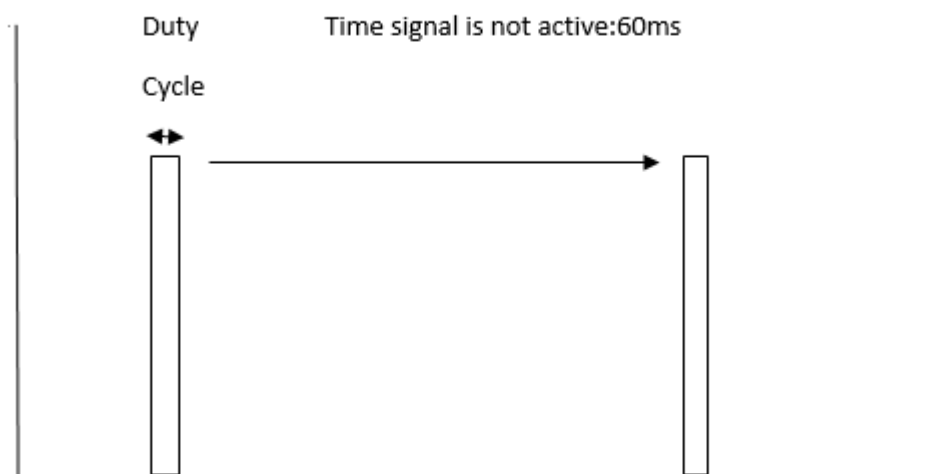


Figure 1: Duty cycle


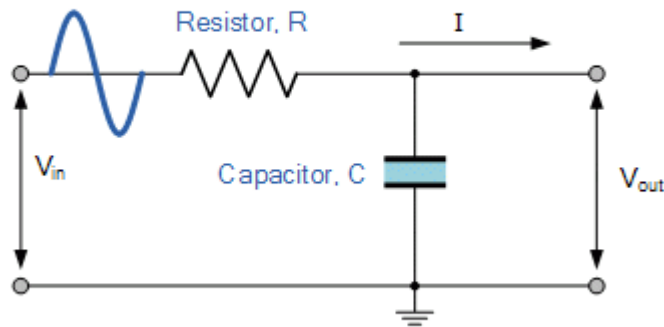


Figure 2: Low pass Filter

PWM signal is a modulation technique to generate different width wave pulses to represent the amplitude of an analog signal.

PWM signals can be transformed by only using a low-pass RC filter(Figure 2).This RC filter will then be directly proportional to the duty cycle of PWM.We want to get rid of the frequency where the signal is not active.In this case the frequency of the signal is 16Hz.The duty cycle of this wave is 0.017 percent.We can then use the time where the signal is not active and with that we can calculated our cut off frequency.We will also need to add an amplifier to amplify signal,because a low pass filter might lower the voltage.Only 0.707 of the voltage gain is able to pass the through the low pass filter.

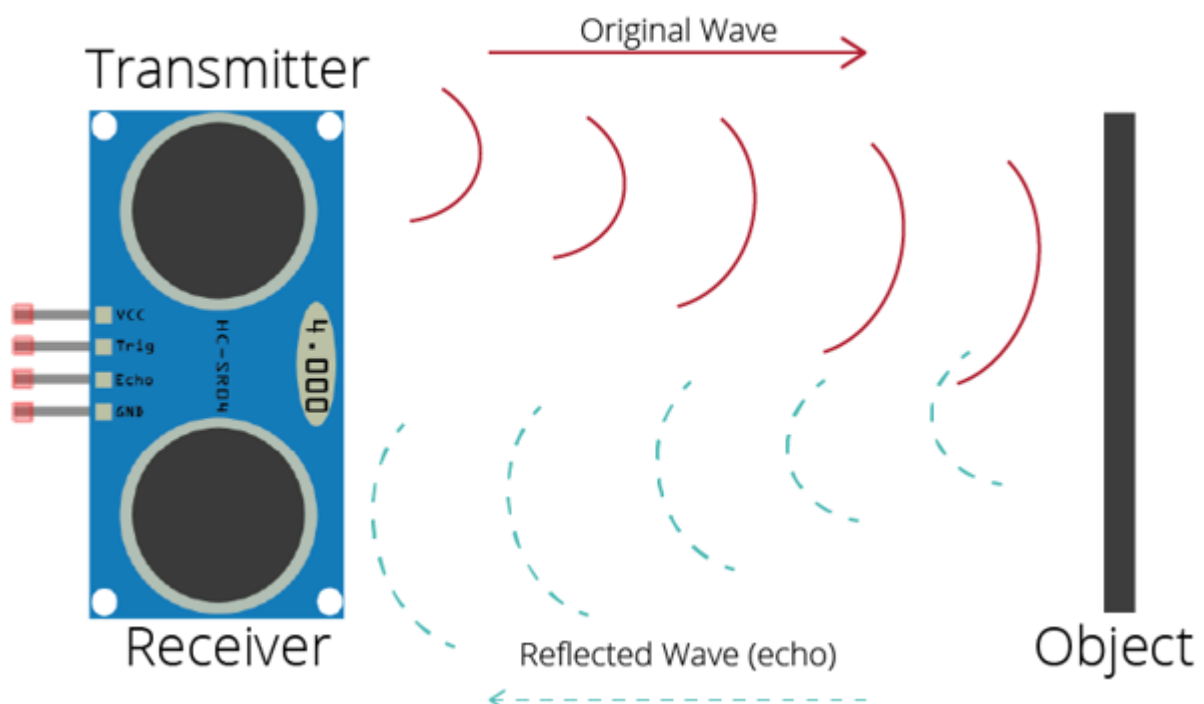1.5. Fundamental operation of the range sensor



The ultrasonic sensor consists of four pins. One of the pins, the trigger pin, is used to trigger a ultrasonic sound wave. This wave will then travel and the pin will stay be set on HIGH for 10us. This will then cause an ultrasonic burst of eight pulses at 40kHz. When this ultrasonic sound wave hits an object it will reflect a signal . This signal will then be received by the ultrasonic sensor which will set the echo pin back to LOW. After the reflected signal has been received the echo pin will then echo a pulse from 25us to 50ms dependent on the time it took for the signal to be received.. The time it takes for the echo pin to stay high will then be used to determine the distance between the ultrasonic sensor and the object.

Chapter 2


Detail design

I had to design an small signal amplifying op-amp, and a low current sensor with a lowpass filter which will then filter all the noise with a cut off frequency of 1kHz.

I used a cut off frequency of 10Hz to cancel all the noise bigger than 10Hz. I used 10Hz, because I said that $f=1/T$ and then calculated the frequency to be 10Hz. The lower your frequency is how lower your amount of noise will be. I will then use this frequency to create a low pass filter. I then used the following equation to calculate the resistance and the value of the capacitor.

numbered equation in Eq. 2.3.

$$f_c = \frac{1}{2\pi CR}. \quad (2.1)$$

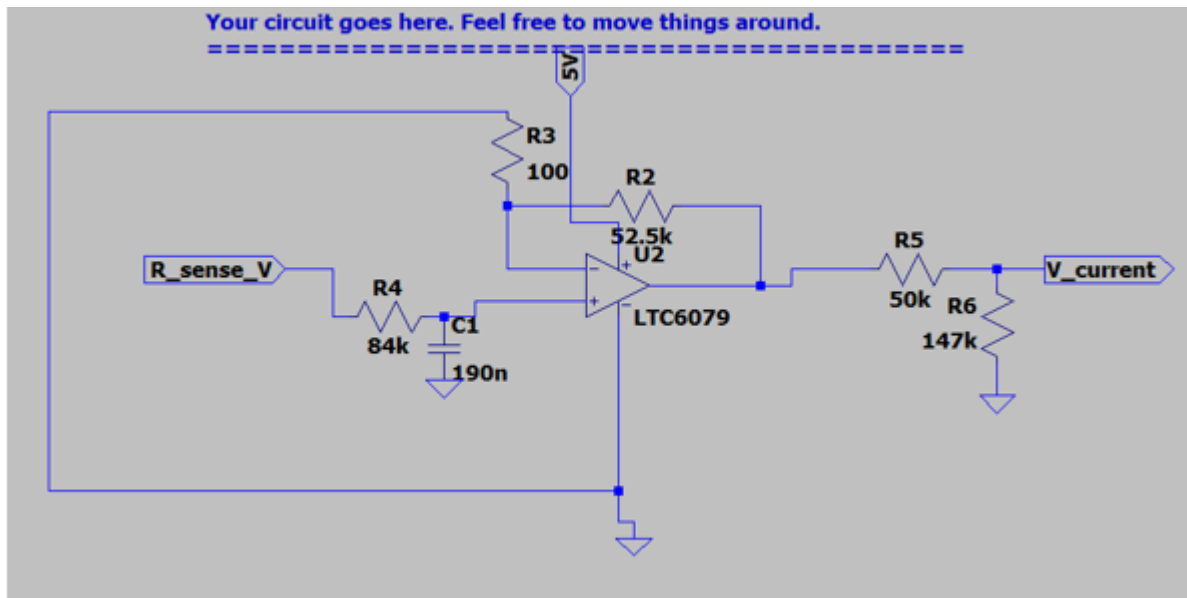

The max current measured over the motor at 6V is 1A. I chose to choose my max current 0.95A. The max voltage that will be entering the op amp will then be 10mV multiplied by the max current. The max voltage will be then 9.5mV. I also chose the output voltage to be 5V at max current. This will then enable me to use voltage division to get my output 3.3V. The Gain will be calculated by this formula:

$$A_v = 1 + \frac{R_2}{R_3}. \quad (2.2)$$


This table will show you the characteristics I needed to consider before designing the op amp

Common mode voltage	Rail voltage	Differential Mode voltage	Expected input voltage	Maximum allowable voltage
0-5V	5.5V	-	10mV	2.7-5.5V

The voltage input of the operational amplifier is 10mV. My rail voltage is 5V and ground which meets the specifications. My output voltage between 3V and 3.6V for that is the only voltages my microprocessor would be able to handle and that is why I made my output voltage to be 3.3V. I used voltage division and calculated the voltage division in the following way:

$$3.3V = 5V \left(\frac{R6}{R5 + R6} \right). \quad (2.3)$$

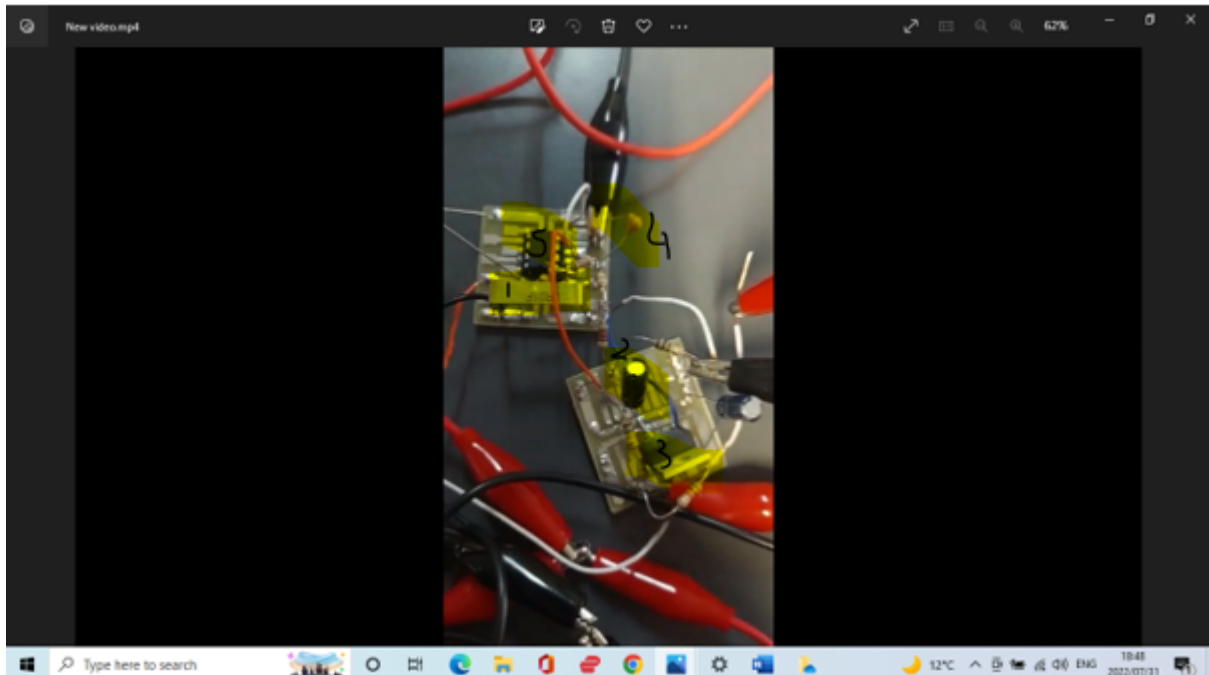
. I used the following resistors: R4=84Kohm R3=100ohm R2=52.5kohm R5=50kohm R6=147kohm



- 1-Rsense(0.1 ohm)
- 2-Capacitors to help with oscillation. Make the voltage stable
- 3-Voltage regulator(7.2V-5V)
- 4-Capacitor for low pass filter.
- 5-Operational amplifier.

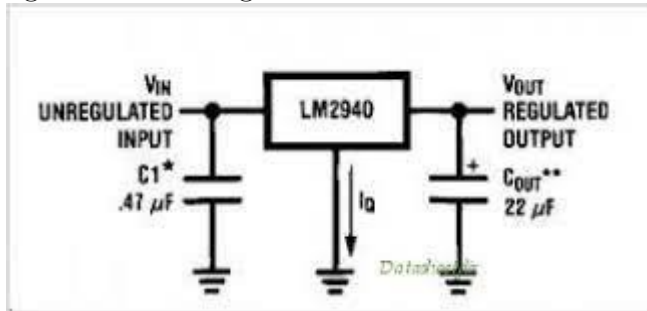2.1. Voltage regulator

My design is according to the datasheet. The Datasheet of the LM2940CT. This design is used to regulate the voltage from 7.2V to 5V.



2.2. Design for ultrasonic sensor

The first thing I had to do was to remove the unwanted signal in the PWM signal. The time where the signal was not active was 60ms. I had to cut out 60ms of the signal where it was not active. I used the following formula to calculate the cut off frequency. The op-amp I will be using in my design is MCP6242. This op-amp uses a common mode input voltage with the range of $V_{dd}+350\text{mV}$, $V_{ss}-300\text{mV}$.

$$f_c = 1 / (2 \times \pi \times 60\text{ms})$$
$$= 2.653\text{Hz}$$


The cut off frequency had to be lower than 2.653Hz. When using this frequency, my signal still had a lot of noise. I lowered my cut off frequency till I reached less noise. The cut off frequency I chose was 0.3Hz. I also chose resistance to be 53kΩ. I calculated the capacitance by using the following formula:

$$f_c = 1 / (2 \times \pi \times R \times C)$$

I calculated the capacitance to be 10μF. I then had to amplify the signal. The output of this signal was equal to 600mV and I wanted it to be 3.3V. To calculate the gain I used the following formula:

$$A_v = R_2 / R_1$$

I chose R_1 to be equal to 100kΩ. I then calculated the R_2 to be 500kΩ. To smooth out the noise on the signal even more I picked a 330nF capacitor. I used this capacitor to lower the noise on the signal down to 70mV peak to peak. In the building of my circuit I will be using 3.3V to power my op-amp, because when my distance measured on my ultrasonic sensor is more than 1 meter, my output voltage is more than 3.3V.

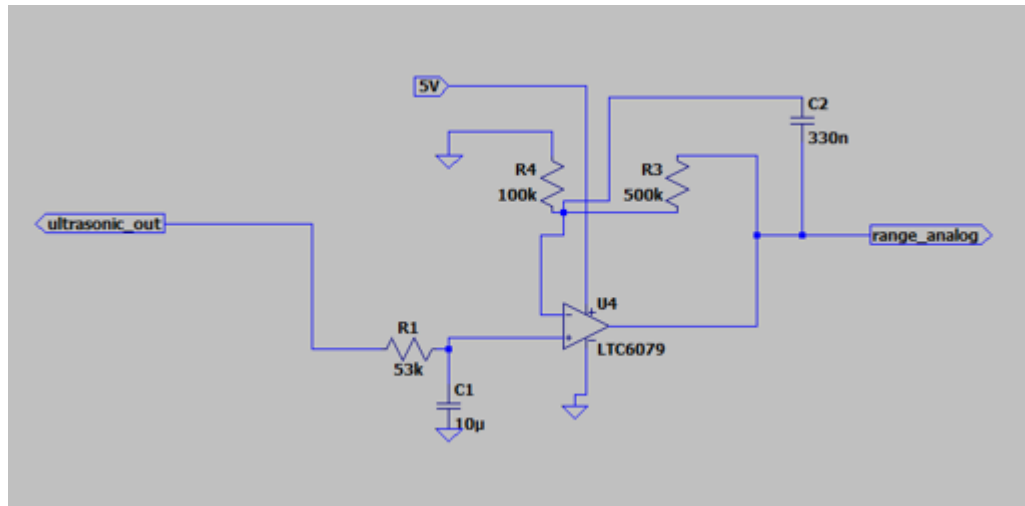

Chapter 3


Results

In this section I will be showing my results by referring to my simulation results and will be showing how my designed circuit behaves. I will also be showing the current use of the DC motor according to it's condition.


Table 3.1: voltage use of circuit when motor:.

stall	running
3.2	0.45 V

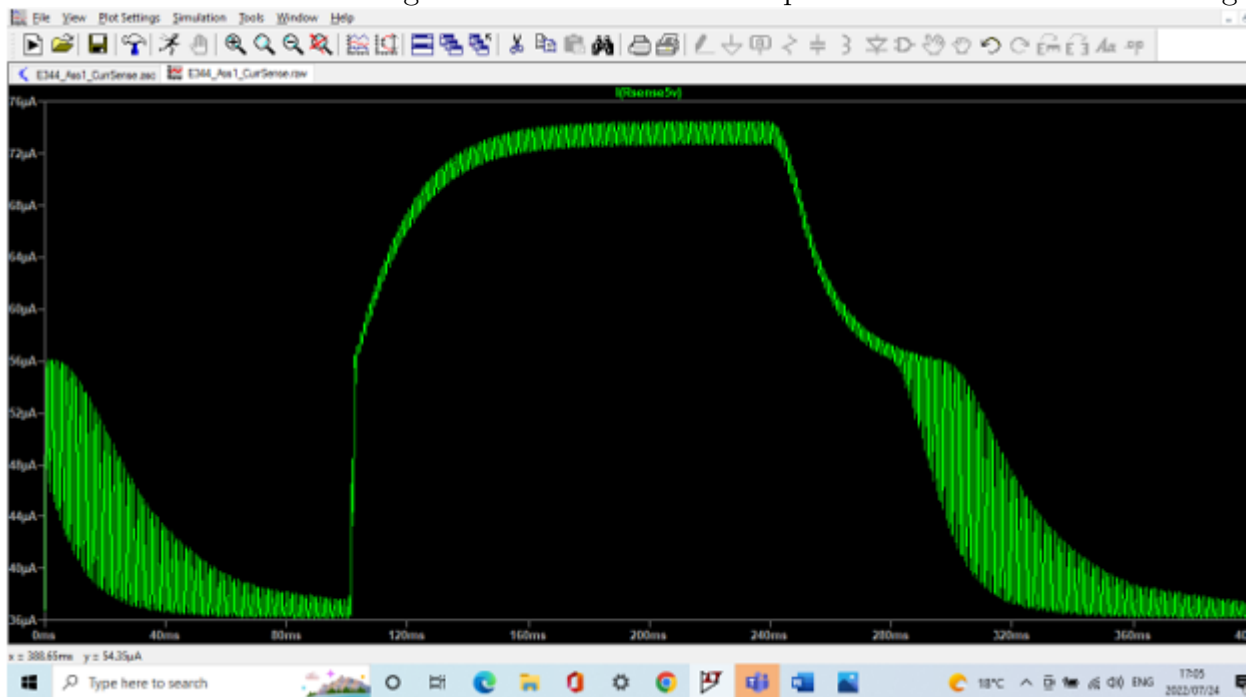
The current through Rsense is equal to the following:




The input with the noise is :

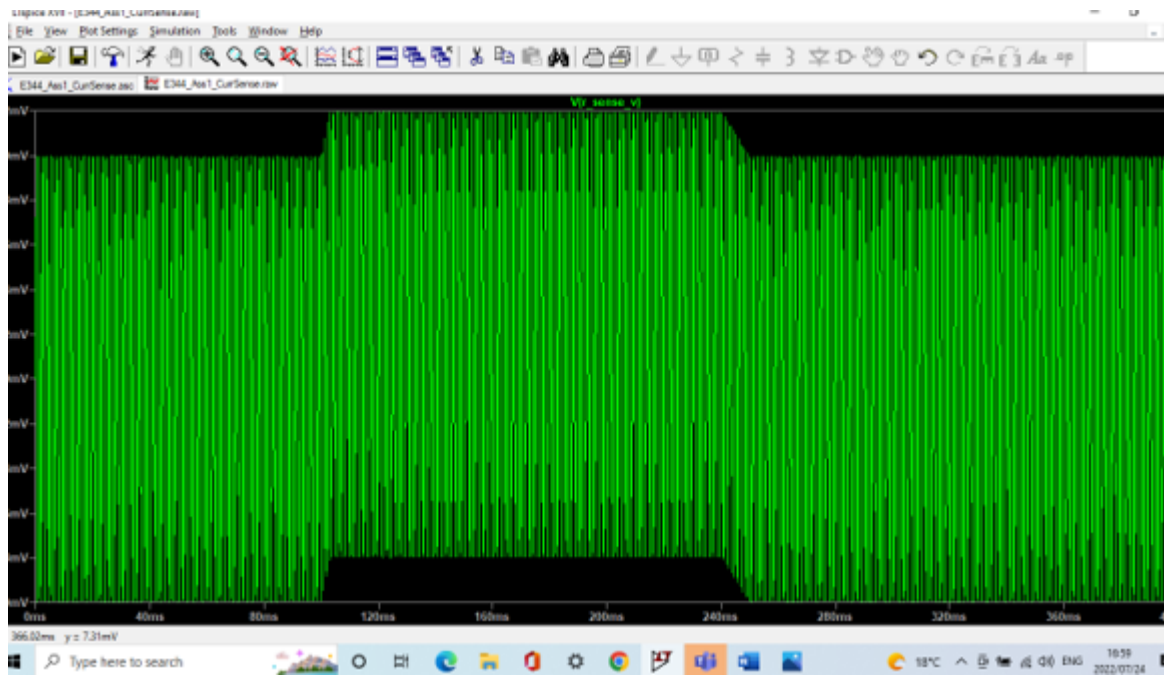


Output without any noise:

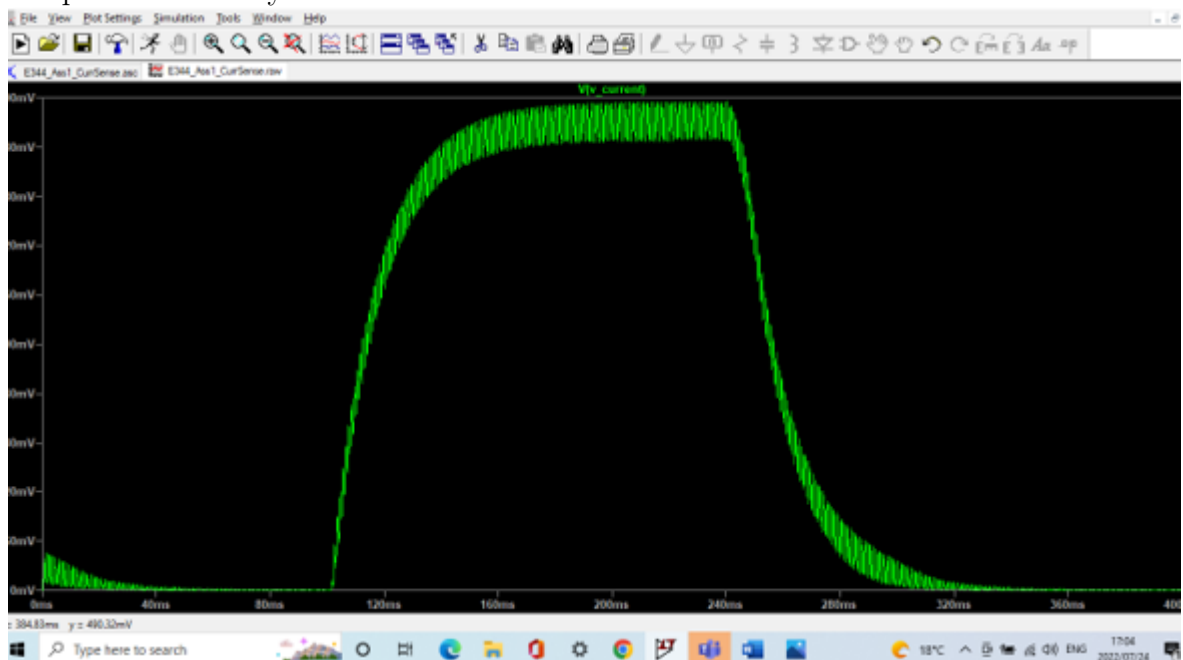

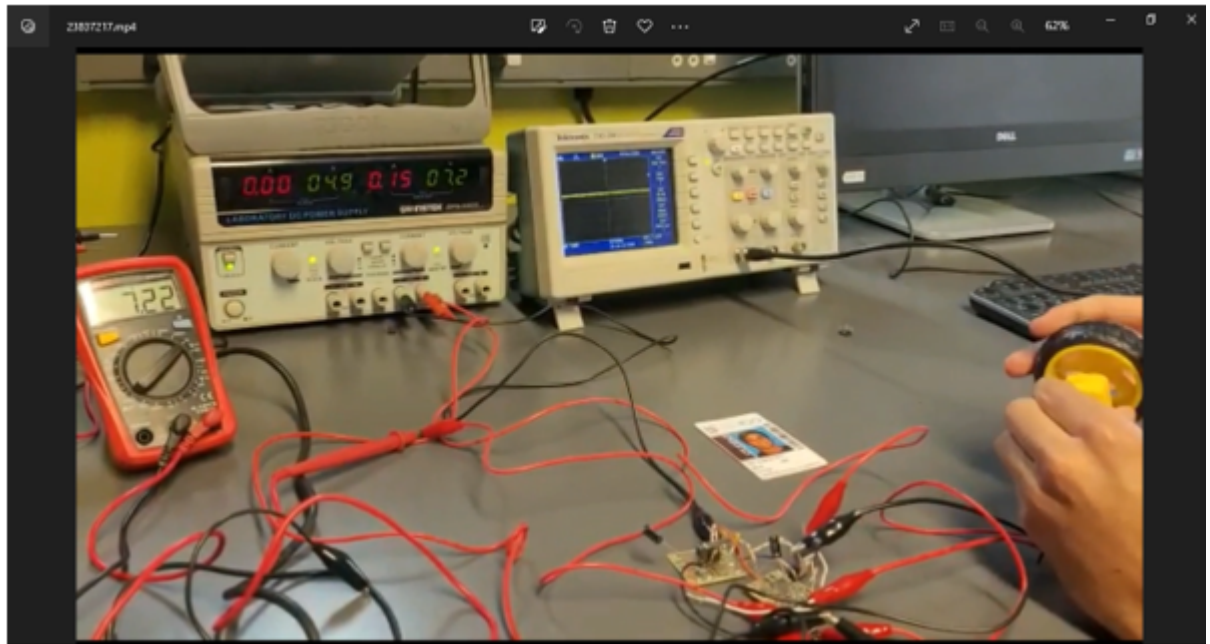Results when 1.5A input and wheel is running:




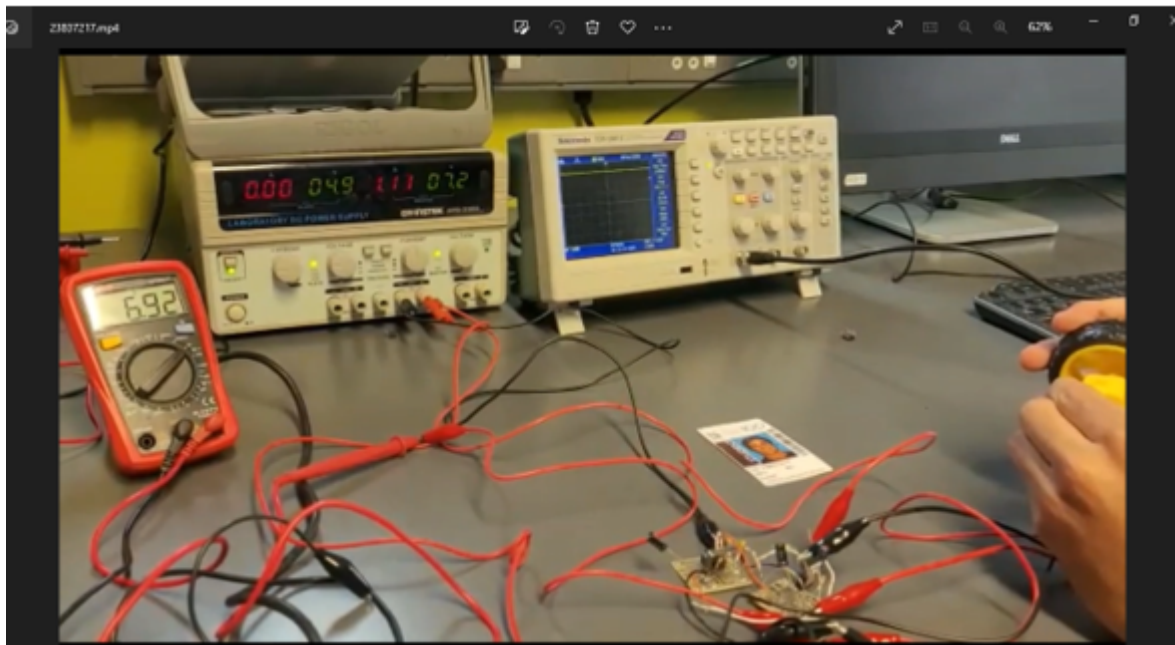Results when 1.5A input and wheel is stalled:




When the input current is 1.5A, the output voltage, when the wheel is stalled, is 3.2V. When current is 0.25A the results remain the same, but when the wheel is stalled the voltage goes down to 0V.

When 0A or 0.05A is input:

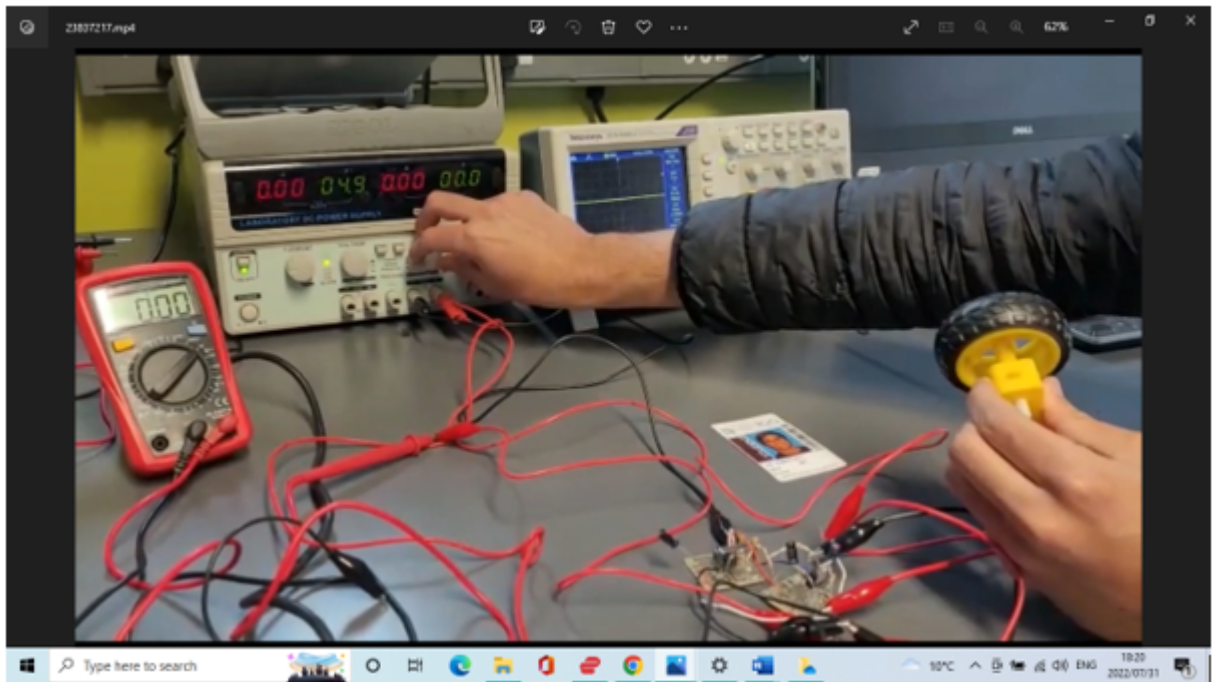


3.1. Ultrasonic sensor design


Output of the signal:

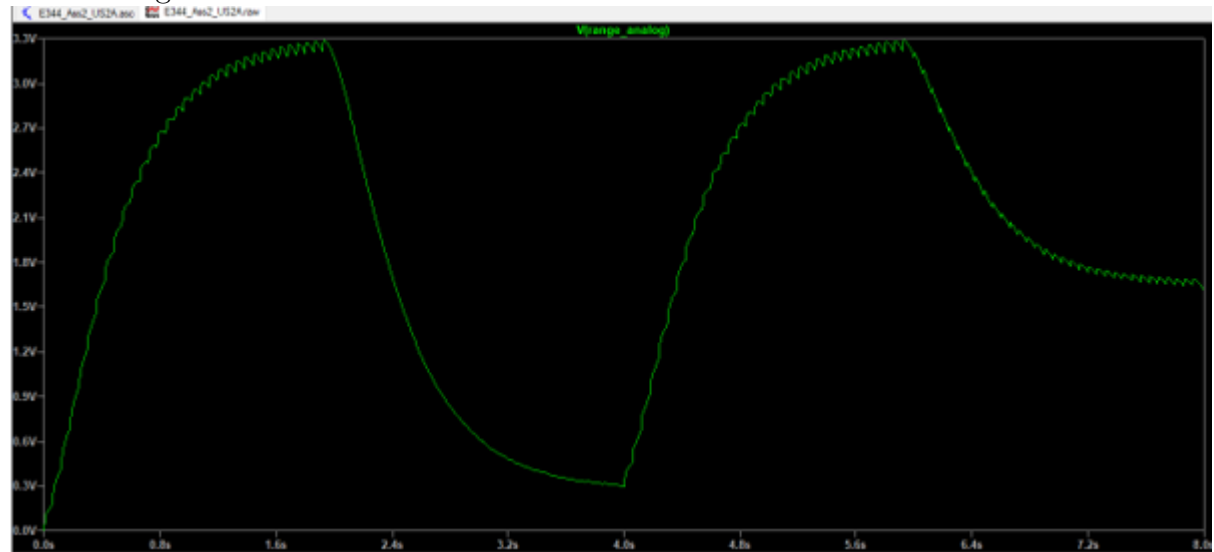

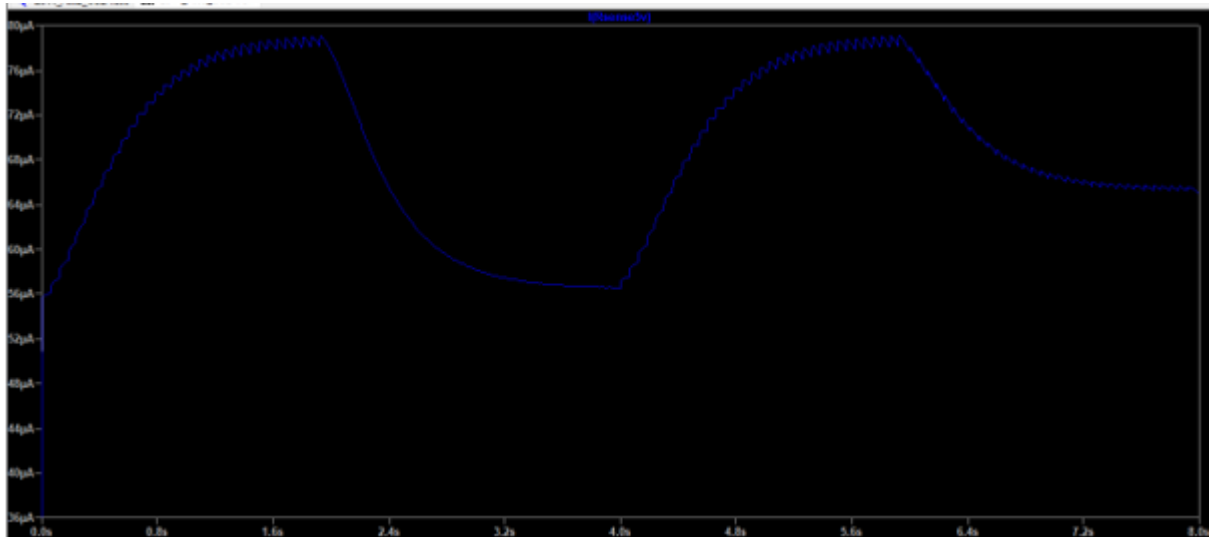
The amount of current going through Rsense:




input of system

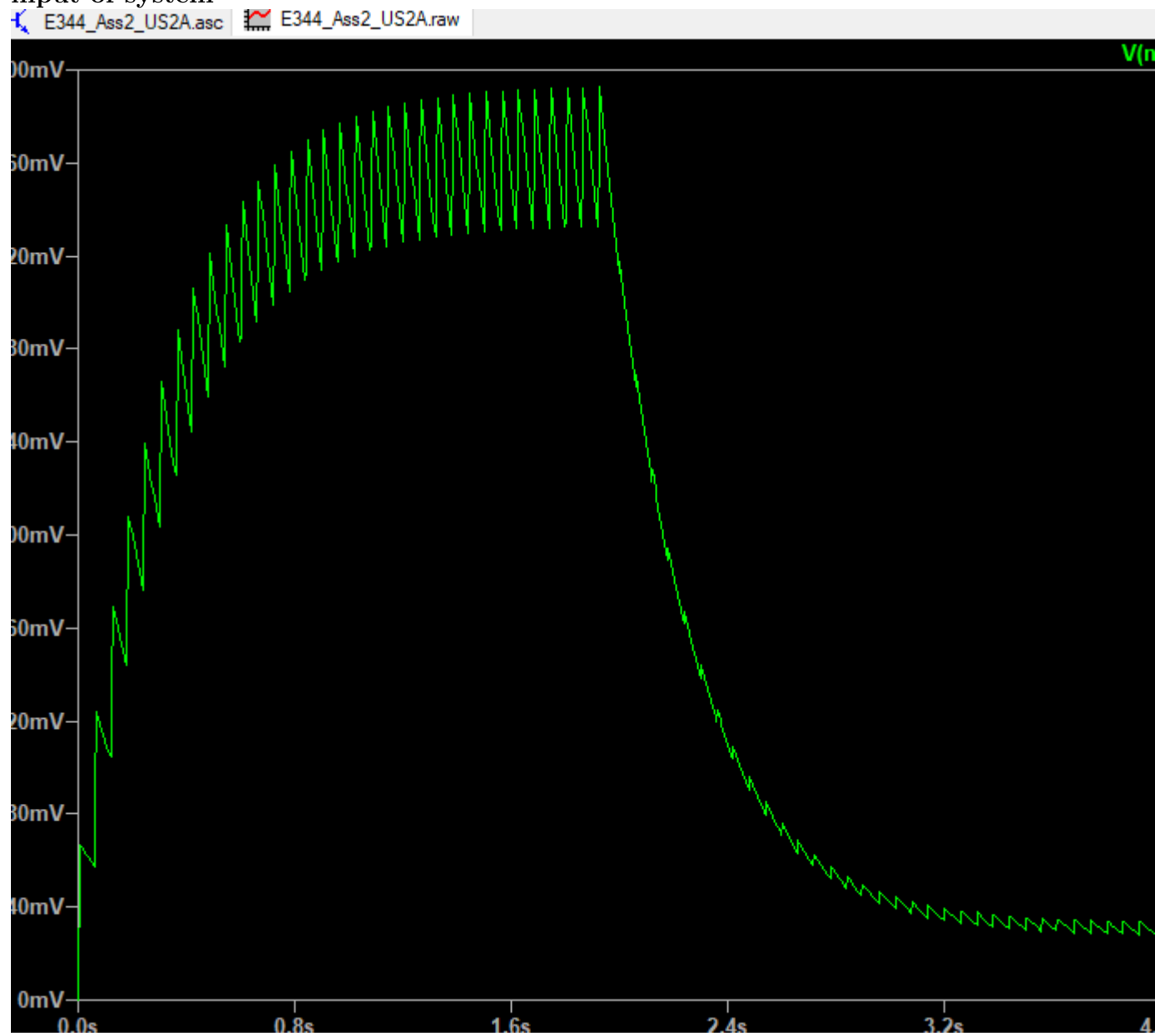

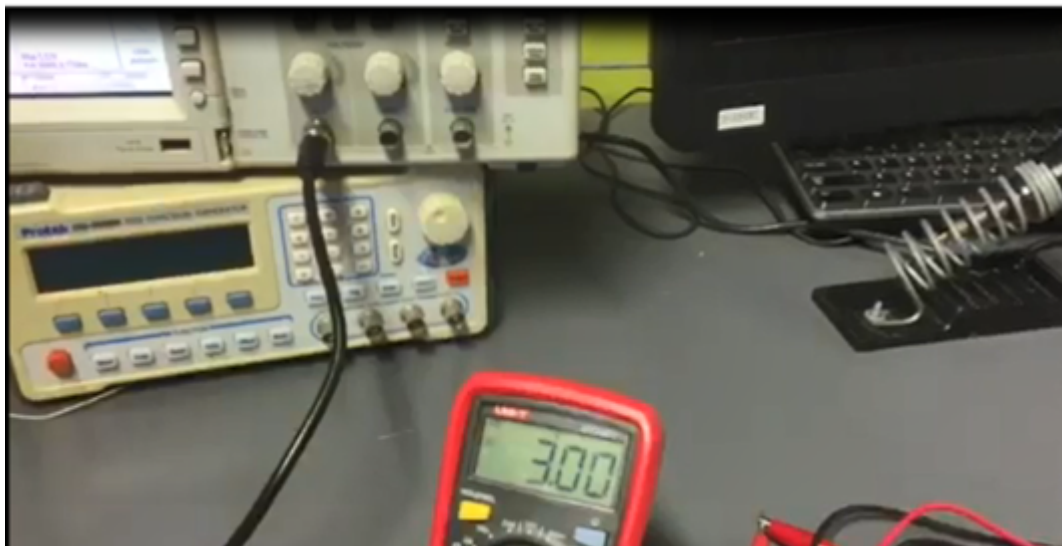Results of practical circuit: Results when 1m away:



Results when closer than 0.05m

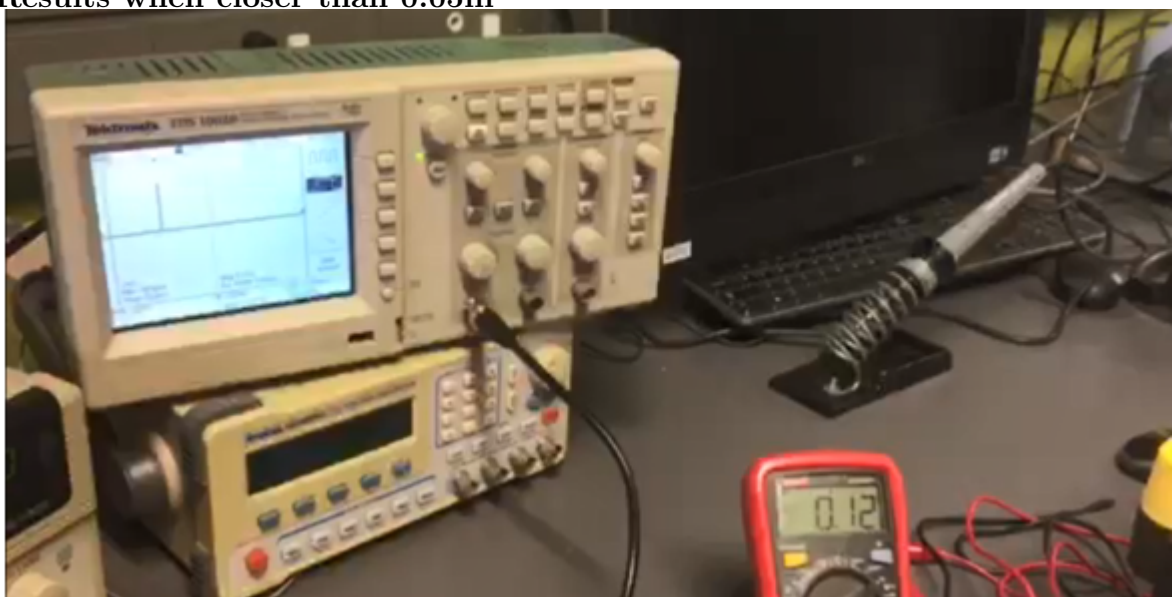

Bibliography

<https://www.allaboutcircuits.com/technical-articles/low-pass-filter-a-pwm-signal-into-an-analog-voltage/>. [Accessed: 07- Aug- 2022].

HC-SR04 Ultrasonic Sensor”, Components101, 2022. [Online]. Available: <https://components101.com/sensors/ultrasonic-sensor-working-pinout-datasheet>. [Accessed: 07- Aug- 2022].

”How HC-SR04 Ultrasonic Sensor Works and How to Interface It With Arduino”, Last Minute Engineers, 2022. [Online]. Available: <https://lastminuteengineers.com/arduino-sr04-ultrasonic-sensor-tutorial/>. [Accessed: 07- Aug- 2022].

Appendix A

Social contract

Download copy from SUNLearn, sign and include here (replace this one).



UNIVERSITEIT-STELLENBOSCH-UNIVERSITY jou kennisvernoot
- your knowledge partner

E-design 344 Social Contract

2022

The purpose of this document is to establish commitment between the student and the organisers of E344. Beyond the commitment made here, it is not binding.

In the months preceding the term, the lecturer (Thinus Booysen) and a few paid helpers (Rita van der Walt, Keegan Huff, and Michael Ritchie) spent countless hours to prepare for E344 to ensure that you get your money's worth, that you are enabled to learn from the module, and demonstrate and be assessed on your skills. We commit to prepare the assignments, to set the assessments fairly, to be reasonably available, and to provide feedback and support as best and fast we can. We will work hard to give you the best opportunity to learn from and pass analogue electronic design E344.

I,Henry Charles Louw..... have registered for E344 of my own volition with the intention to learn of and be assessed on the principals of analogue electronic design. Despite the potential publication online of supplementary videos on specific topics, I acknowledge that I am expected to attend the scheduled lectures to make the most of these appointments and learning opportunities. Moreover, I realise I am expected to spend the additional requisite number of hours on E344 as specified in the yearbook.

I acknowledge that E344 is an important part of my journey to becoming a professional engineer, and that my conduct should be reflective thereof. This includes doing and submitting my own work, working hard, starting on time, and assimilating as much information as possible. It also includes showing respect towards the University's equipment, staff, and their time.

Prof. MJ (Thinus) Booysen

Student number:23837217.....

Signature:..... Date:

Date:22/07/24.....

Appendix B

GitHub Activity Heatmap

